

SINGLE AND TWO CAPACITOR (SOLENOID) PARADOX (STUDIED AT THE REALISTIC CIRCUITS)

Vladan Panković

Department of Physics, Faculty of Sciences, 21000 Novi Sad, Trg Dositeja
Obradovića 4

PACS number: **41.20-q**

Abstract

We study remarkable two (single) capacitor paradox and we introduce analogously a new two solenoids (inductive coils) paradox at experimentally and theoretically well-known electrical circuits with realistic electrical resistances. Electrical field energy “loss” (capacitors) or magnetic field energy “loss” or “creation” (solenoids) can be consistently and consequently described by the well-known work by movement of the electrical charge in the electrical field (capacitors) or by well-known work of the electrical currents (solenoids) without any additional dissipative processes.

1. SINGLE AND TWO CAPACITOR PARADOX

As it is well-known remarkable two-capacitors paradox, formulated and considered in many textbooks and articles on the basic principles and applications of the electronic and electrodynamics [1]-[7], states the following. Consider an ideal (without any electrical resistance and inductivity) electrical circuit with first, initially charged, and second, initially non-charged, of two identical capacitors. In given circuit, by transition from initial, open state (switch OFF state) in the closed state (switch ON state), an unexpected, mysterious loss of the half of initial energy of electrical fields within capacitors occurs. Different authors [4]-[7] suggest that given energy loss is realized by different dissipative processes (Joule heating or/and electromagnetic waves emissions) realized by non-neglectable residual electric resistances and inductivities in realistic circuits. On other words seemingly paradoxical conclusions of the original formulation of the paradox here are consequence of the non-admittable simplifications of the realistic processes that occurs in the electrical circuits.

In this work, firstly, single capacitor paradox will be considered. Precisely we shall consider mentioned single capacitor paradox at *theoretically and experimentally well-known realistic model of the single capacitor discharge* by connection of capacitor plates using conductive wire and switch with *realistic electrical resistance*. Here after transition from open state (switch OFF position) in the closed state (switch ON position), *theoretically and experimentally unambiguous and well-known exponential discharge* of the capacitor occurs as well as corresponding *total* loss of the initial energy of the electrical field between capacitor

plates. Given energy loss will be *simply and consistently* explained by work of the electrical field by movement of the electric charge from one in the other plate of the capacitor. Here electrical resistance has no any explicit role and in this sense it (as well as different dissipative processes, e.g. Joule heating or/and electromagnetic waves emissions) can be effectively neglected. Two capacitors paradox will be explained in the analogous way. Here given energy loss will be *simply and consistently* explained by work of the electrical field by movement of the electric charge from one in the other the capacitor. Also, here electrical resistance has no any explicit role and in this sense it (as well as different dissipative processes, e.g. Joule heating or/and electromagnetic waves emissions) can be effectively neglected. Finally, we shall introduce and solve in the analogous way a new paradox, paradox of two solenoids (inductive coils) with *realistic electrical resistance*. Here *seeming loss or creation of the energy of magnetic field corresponds to the well-known work of the electrical currents (difference) through solenoids so that here, also, different dissipative processes, e.g. Joule heating or/and electromagnetic waves emissions can be effectively neglected, moreover (by energy creation) impossible.*

Consider, firstly, theoretically and experimentally well-known realistic model of the single capacitor discharge. Precisely consider a simple electrical circuit with single charged capacitor with the capacitance C and one switch.

Initially, switch is in the state OFF so that electrical circuit is open. Then capacitor is charged by electrical charge Q and holds voltage $V=Q/C$. Initial energy of the electric field within capacitor equals, as it is well-known,

$$(1) \quad E_{in} = CV^2/2 = Q^2/(2C)$$

When switch turns out in the state ON electrical circuit becomes closed. Suppose that conductive wire that connects opposite plates of the capacitor holds some non-zero electric resistance R . Also, it will be supposed that in mentioned closed circuit there is no any additional voltage sources.

Then, as it is well-known, according to the second Kirchhoff rule (that represents immediate consequence of the *energy conservation law!*) it follows

$$(2) \quad q/C + R dq/dt = 0$$

where q represents the capacitor electrical charge in the time moment t , while dq/dt represents electrical current through circuit in the same moment. Simple integration of this equation yields

$$(3) \quad q \equiv q(t) = q(0) \exp [-t/(RC)] = Q \exp [-t/\tau]$$

where $q(0) = Q$ represents the initial electrical charge of the capacitor while

$$(4) \quad \tau=RC$$

represents the characteristic time of the capacitor discharge. Obviously, τ is directly proportional to R , so that τ is large for large R and vice versa τ is small for small R . In any case q decreases exponentially during time so that τ can be roughly treated as the discharge time (exactly speaking total discharge of the capacitor needs infinite time)..

In arbitrary time moment t energy of the electric field between capacitor plates equals

$$(5) \quad E(t)= Cv^2(t) /2 = q^2(t)/(2C)$$

where

$$(6) \quad v(t) = q(t) /C$$

represents the voltage between capacitor plates in the time moment t .

All this implies that after discharge time both, voltage between capacitor plates and energy of the electric field between capacitor plates, become finally practically zero, i.e.

$$(7) \quad v(t \geq \tau) \approx 0$$

$$(8) \quad E_{fin} \equiv E(t \geq \tau) \approx 0$$

where E_{fin} represents the final energy of the electrical field between capacitor plates.

In this way there is the following electrical field energy discrete difference between the final and initial state of given electrical circuit

$$(9) \quad \Delta E = E_{\text{fin}} - E_{\text{in}} = - Q^2/(2C) \quad .$$

It seems as a paradoxical total energy loss.

Now we shall explain what this energy loss really represents.

Total differential of (5) and (6) yield

$$(10) \quad dE(t) = C dv(t) \quad v(t) = dq(t) \quad v(t) \quad .$$

Here expression

$$(11) \quad dA(t) = dq(t) \quad v(t)$$

,according to well-known definition of the work in the electrical field, can be considered as the work done by capacitor electrical field by movement of the electrical charge $dq(t)$ from one capacitor plate in the other with corresponding voltage $v(t)$ in the time moment t .

In this way it follows

$$(12) \quad dE(t) = dA(t)$$

which means that differential change (decrease) of the energy of the electrical field between capacitor plate is identical to the differential work done by the electrical field by transition of the differential electrical charge from the one capacitor plate to the other.in given time moment.

It is very important to be pointed out that none of the expressions (5), (6), (10), (11), (12) is explicitly time (or resistance) dependent. It admits simple integration of (12) in form

$$(13) \quad A = E_{\text{fin}} - E_{\text{in}} = \Delta E = - Q^2/(2C) \quad .$$

which implies

$$(14) \quad \Delta E = A \quad .$$

It means that *mentioned energy loss is identical to total work of the capacitor time variable electrical field by total electrical charge movement from one into other capacitor plate* (equivalent to the capacitor discharge). *It is all and nothing more is necessary.*

Especially, electric resistance R , that determines explicitly time of the capacitor discharge, *has no any explicit influence* on the basic nature (work by mentioned electric charges movement) of the electric field energy loss. In this sense *really existing* electric resistance can be *effectively neglected*. *Obviously it refers on the other different dissipative processes (Joule heating or/and electromagnetic waves emissions) too.*

Consider now two capacitor paradox at the analogs realistic model of the two capacitors discharge.

Precisely consider a simple electrical circuit with two capacitors with the same capacitance C and one switch.

Initially, switch is in the state OFF so that electrical circuit is open. A;so, first capacitor is charged by electrical charge Q and holds voltage $V=Q/C$. Simultaneously second capacitor is discharged. Initial total energy of the electric field within both capacitors equals, as it is well-known,equals

$$(15) \quad E_{\text{in}} = CV^2/2 = Q^2/(2C)$$

When switch turns out in the state ON electrical circuit becomes closed. Suppose that conductive wires that connect capacitors hold some non-zero electric resistance R . Also, suppose that in mentioned closed circuit there is no additional voltage sources.

Then, as it is well-known, according to the second Kirchoff rule (that represents immediate consequence of the *energy conservation law!*) it follows

$$(16) \quad (q_1 - q_2)/C + R d(q_1 - q_2)/dt = 0$$

where q_1 and q_2 represent first and second capacitor electrical charge in the time moment t , while $d(q_1 - q_2)/dt$ represents electrical current through circuit in the same moment. Simple integration of this equation yields

$$(17) \quad (q_1 - q_2) = (q_1(0) - q_2(0)) \exp [-t/(RC)] = Q \exp [-t/\tau]$$

where $q_1(0) = Q$ represents the initial electrical charge of the first capacitor while $q_2(0)=0$ represents initial charge of the second capacitor . Also

$$(18) \quad \tau=RC$$

represents the characteristic time of the capacitors charges equivalence. Obviously, τ is directly proportional to R , so that τ is large for large R and vice versa τ is small for small R . In any case $(q_1 -q_2)$ decreases exponentially during time so that τ can be roughly treated as the capacitors charges equivalence time (exactly speaking total equivalence of the capacitors charges needs infinite time)..

According to electrical charge conservation law

$$(19) \quad q_1+q_2 = Q$$

and previous discussion it follows

$$(20) \quad q_1(t \geq \tau) \approx q_2(t \geq \tau) \approx Q/2 \quad \dots$$

In arbitrary time moment t total energy of the electric field between both capacitor plates equals

$$(21) \quad E(t)= q_1^2(t)/(2C) + q_2^2(t)/(2C) \quad \dots$$

All this implies that after τ total energy of the electric field between both capacitor plates, become finally practically

$$(22) \quad E_{fin} \equiv E(t \geq \tau) = 1/2 Q^2/(2C) = 1/2 E_{in} \quad \dots$$

In this way there is the following energy discrete difference between the initial and final state of given electrical circuit

$$(23) \quad \Delta E = E_{fin} - E_{in} = - 1/2 E_{in} = - 1/2 Q^2/(2C) \quad \dots$$

It seems as a paradoxical total energy loss.

Now we shall explain what this energy loss really represents.

Since Q represents a constant, total differential of (19) and (21) yield

$$(24) \quad dq_1 = -dq_2$$

$$(25) \quad dE(t) = dq_1 (q_1 -q_2)/C$$

Here expression

$$(26) \quad dA(t) = dq_1 (q_1 -q_2)/C$$

,according to well-known definition of the work in the electrical field, can be considered as the work done by oppositely directed two capacitors electrical fields by movement of the electrical charge $dq_1(t)$ from one capacitor in the other capacitor with corresponding voltage $(q_1 -q_2)/C$ in the time moment t .

In this way it follows

$$(27) \quad dE(t) = dA(t)$$

which means that differential change (decrease) of the energy of the total electrical field between two capacitors is identical to the differential work done by oppositely directed electrical fields by transition of the differential electrical charge from the one capacitor to the other capacitor in given time moment.

It is very important to be pointed out that none of the expressions (21), (22), (23), (24), is explicitly time (or resistance) dependent. It admits simple integration of (25) in form

$$(28) \quad A = E_{fin} - E_{in} = \Delta E = - 1/2 Q^2/(2C) \quad \dots$$

which implies

$$(29) \quad \Delta E = A \quad \dots$$

It means that *mentioned energy loss is identical to total work of the two capacitors time variable oppositely directed electrical fields by total electrical charge movement from one into other capacitor plate. It is all and nothing more is necessary.* Especially, electric resistance R , that determines explicitly time τ , *has no any explicit influence* on the basic nature (work by mentioned electric charges movement) of the total electric field energy loss. In this sense *really existing* electric resistance can be *effectively neglected*. Obviously it refers

on the other different dissipative processes (Joule heating or/and electromagnetic waves emissions) too.

2. TWO SOLENOIDS (INDUCTIVE COILS) PARADOXES

Consider now two realistic identical solenoids or inductive coils which hold inductivity L and electrical resistance R connected parallel. When a corresponding switch is in OFF state a constant electrical current I goes through the first solenoid only. But when switch is in ON state, according to the first Kirchhoff rule and equivalence of the solenoids, electrical current through any solenoid equals $I/2$. According to the well-known expression for solenoid magnetic field energy, total energy of the magnetic field of both solenoids equals in OFF state

$$(30) \quad E_{\text{OFF}} = LI^2/2$$

while in ON state this energy equals

$$(31) \quad E_{\text{ON}} = L(I/2)^2/2 + L(I/2)^2/2 = (1/2) LI^2/2 = (1/2) E_{\text{OFF}} .$$

It simply implies

$$(32) \quad E_{\text{ON}} - E_{\text{OFF}} = - (1/2) E_{\text{OFF}}$$

and

$$(33) \quad E_{\text{OFF}} - E_{\text{ON}} = (1/2) E_{\text{OFF}} .$$

When switch is firstly in OFF state and latter it turns in the ON state a paradoxical magnetic field energy loss or “half-annihilation” described by (32) occurs. (As it is not hard to see this energy loss corresponds in some way to the energy loss by two capacitor paradox.) But when switch is firstly in ON state and later it turns in OFF state a (even more) paradoxical magnetic field energy “half-creation” described by (33) occurs. (As it is not hard to see mentioned “half-creation” of the magnetic field energy has no any correspondence by any variation of the two capacitor paradox.) Moreover, if there is a periodical change of two switch states there is corresponding periodic change of the “half-annihilation” and “half-creation” of the magnetic field energy (without any analogy with any variation of two capacitor paradox).

Now we shall explain mentioned paradoxical conclusions.

By transition from OFF in ON switch state there are currents i_1 and i_2 trough first and second solenoid. These currents satisfy Kirchhoff first rule

$$(34) \quad I = i_1 + i_2$$

and Kirchhoff second rule

$$(35) \quad Ri_1 + L di_1/dt - Ri_2 - L di_2/dt = 0$$

with initial conditions

$$(36) \quad i_1(0) = I$$

$$(37) \quad i_2(0) = 0 .$$

Expression (35) can be transformed in the following equivalent form

$$(38) \quad R(i_1 - i_2) + L d(i_1 - i_2)/dt = 0$$

with solution

$$(39) \quad (i_1 - i_2) = (i_1(0) - i_2(0)) \exp [-t R/L] = I \exp [-t R/L] ..$$

It means than difference between i_1 and i_2 exponentially decreases during time so that , after characteristic time interval

$$(40) \quad \tau_{12} = L/R$$

, this difference becomes practically zero, while, according to (34) it follows.

$$(41) \quad i_1 = i_2 = I/2 .$$

Expression (34) and (39) imply

$$(42) \quad i_1 = I(1 + \exp [-t R/L])/2$$

$$(43) \quad i_2 = I[1 - (1 + \exp [-t R/L])/2] .$$

In arbitrary time moment t energy of the magnetic field within both solenoids, as it is well-known, equals

$$(44) \quad E(t) = Li^2_1/2 + Li^2_2/2$$

with initial value E_{OFF} and effective final value E_{ON} .

Differential change of (44) equals

$$(45) \quad dE(t) = i_1 L di_1 + i_2 L di_2 = i_1 v_1 dt + i_2 v_2 dt = dA(t) \quad .$$

Here v_1 and v_2 represent voltages at first and second solenoid, while, of course, $dA(t)$ represent differential total work of both electrical currents through the first and second solenoid

Since I represents a constant differentiation of (34) yields

$$(46) \quad di_2 = -di_1$$

, which, introduced in (45), yields

$$(47) \quad dE(t) = i_1 L di_1 - i_2 L di_1 = (i_1 - i_2) v_1 dt \quad . \quad .-$$

It, obviously, can be considered as the work of the difference of the electrical currents through first and second solenoid by voltage v_1 .

As it is not hard to see after integration of (45) over whole t total change of the magnetic field energy is described by (32) corresponding to mentioned energy loss or “half-annihilation” on the one hand, and, on the other hand, it represents total work of the electrical currents (differences) through solenoids.

It is all and nothing more is necessary. Especially, electric resistance R determines numerically mentioned energy loss but this resistance *has no any explicit influence* on the basic nature (work of the electrical currents) of this energy loss. In this sense *really existing* electric resistance can be *effectively neglected*. Obviously it refers on the other different dissipative processes (Joule heating or/and electromagnetic waves emissions) too.

Dynamics by transition from ON in OFF state is described by (34) and the following second Kirchhoff rule

$$(48) \quad Ri_2 + L di_2/dt = 0$$

with initial condition

$$(49) \quad i_2(0) = I/2 \quad .$$

It yields

$$(50) \quad i_2 = I/2 \exp [-t R/L]$$

$$(51) \quad i_1 = I (1 - 1/2 \exp [-t R/L]) \quad .$$

Here time interval, numerically identical to (40) can be considered as the effective time of the i_2 disappearance.

Dynamics of the change of the energy of the magnetic fields is again given by expressions (44)-(47) so that total change of the magnetic field energy can be again explained as the total work of the electrical currents (differences). But here this energy change is expression corresponding to (33) formally called energy “half-creation”.

It is all and nothing more is necessary. Especially, electric resistance R determines numerically mentioned energy “half-creation”. but this resistance *has no any explicit influence* on the basic nature (work of the electrical currents) of this energy “half-creation”.. In this sense *really existing* electric resistance can be *effectively neglected*. Obviously it refers on the other different dissipative processes (Joule heating or/and electromagnetic waves emissions) too. (It can be added the following. In theories that would attempt to explain magnetic energy loss paradox using some emission processes, magnetic energy “half-creation” paradox needs spooky or impossible absorption processes.)

Finally, as it is not hard to see, all previous explanations can be simply generalized in case of the periodic change of “half-annihilation” and “half-creation” of magnetic field energy by corresponding periodical change of two switch states

3. CONCLUSIONS

In conclusion, the following can be shortly repeated and pointed out. In this work, firstly, single capacitor paradox is considered. Precisely we consider mentioned single capacitor paradox at *theoretically and experimentally well-known realistic model of the single capacitor discharge* by connection of capacitor plates using conductive wire and switch with *realistic electrical resistance*. Here after transition from open state (switch OFF position) in the closed state (switch ON position), *theoretically and experimentally unambiguous and well-known exponential discharge* of the capacitor occurs as well as corresponding *total* loss of the initial energy of the electrical field between capacitor plates. Given energy loss is *simply and consistently* explained by *work of the electrical field by movement of the electric charge from one in the other plate of the capacitor*. Here electrical resistance *has no any explicit role* and in this sense *it (as well as different dissipative processes, e.g. Joule heating or/and electromagnetic waves emissions) can be effectively neglected*. Two capacitors paradox is explained in the analogous way. Here given energy loss is *simply and consistently* explained by *work of the electrical field by movement of the electric charge from one in the other the capacitor*. Also, here electrical resistance *has no any explicit role* and in this sense *it (as well as different dissipative processes, e.g. Joule heating or/and electromagnetic waves emissions) can be effectively neglected*. Finally, we introduce and solve in the analogous way a new paradox, paradox of two solenoids (inductive coils) with *realistic electrical resistance*. Here *seeming loss or creation of the energy of magnetic field corresponds to the well-known work of the electrical currents (difference) through solenoids so that here, also, different dissipative processes, e.g. Joule heating or/and electromagnetic waves emissions can be effectively neglected, moreover (by energy creation) impossible*.

References

- [1] D. Halliday, R. Resnick, *Physics, Vol. II* (J. Willey, New York, 1978)
- [2] F. W. Sears, M.W. Zemansky, *University Physics* (Addison-Wesley, Reading, MA, 1964)
- [3] M. A. Plonus, *Applied Electromagnetics*, (McGraw-Hill, New York, 1978)
- [4] E. M. Purcell, *Electricity and Magnetism, Berkeley Physics Course Vol. II* (McGraw-Hill, New York, 1965)
- [5] R. A. Powel, *Two-capacitor problem: A more realistic view*, Am. J. Phys. **47** (1979) 460
- [6] T. B. Boykin, D. Hite, N. Singh, Am. J. Phys. **70** (2002) 460
- [7] K. T. McDonald, *A Capacitor Paradox*, class-ph/0312031